



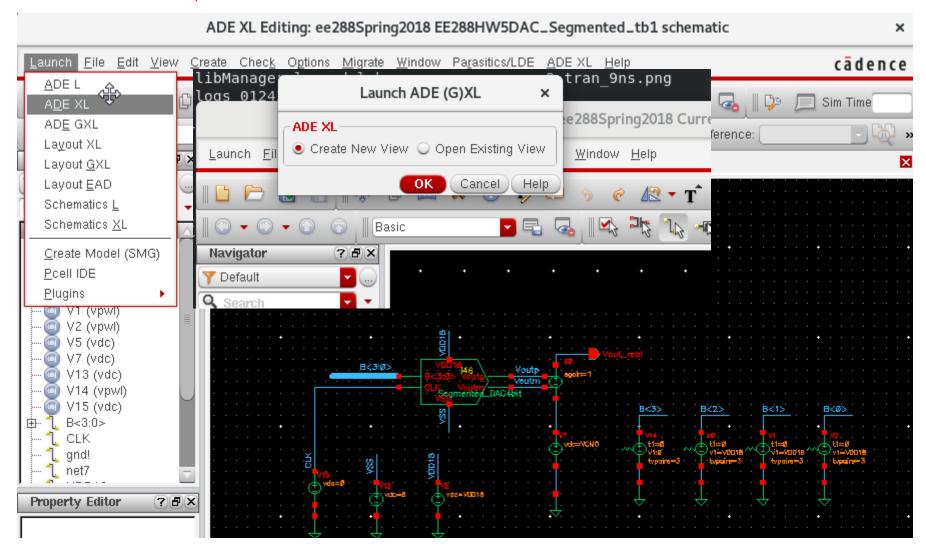
In Schematic View, Launch ADE XL and choose Create New View



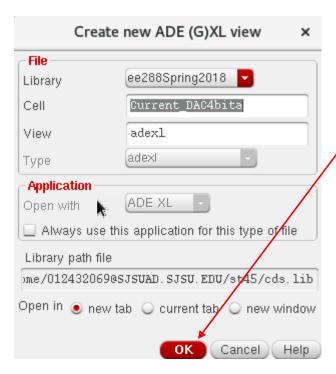


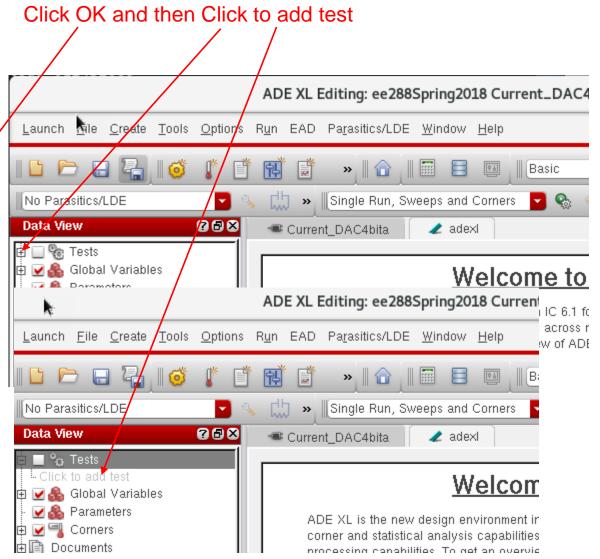


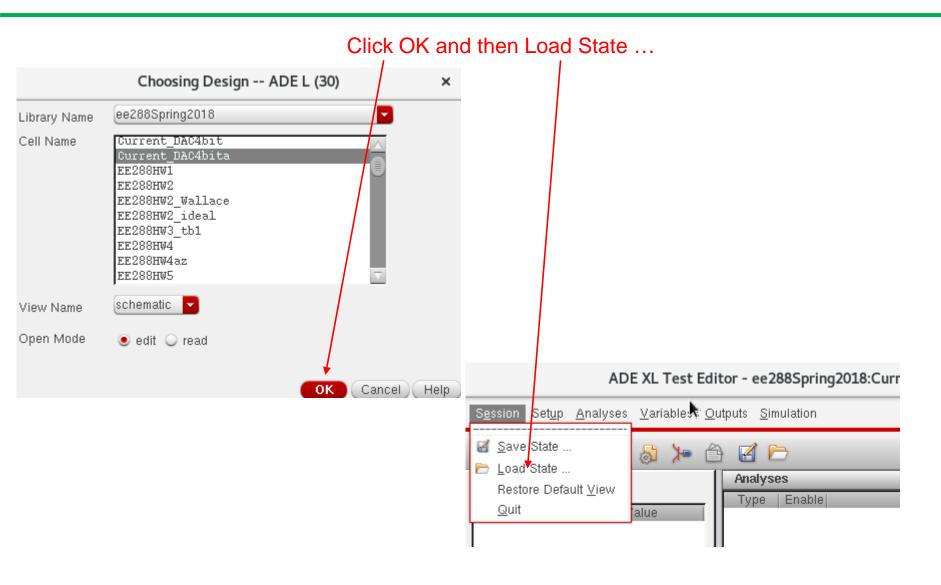

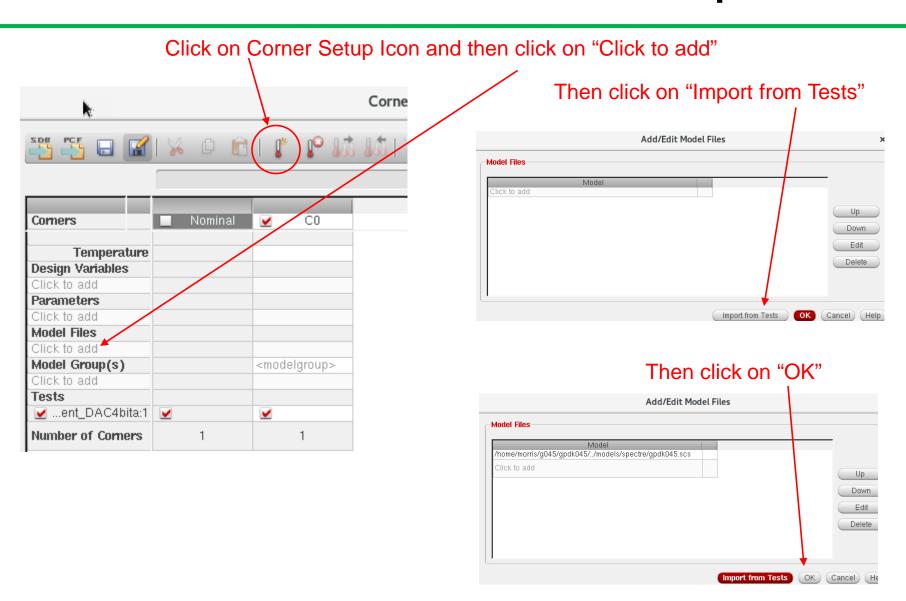


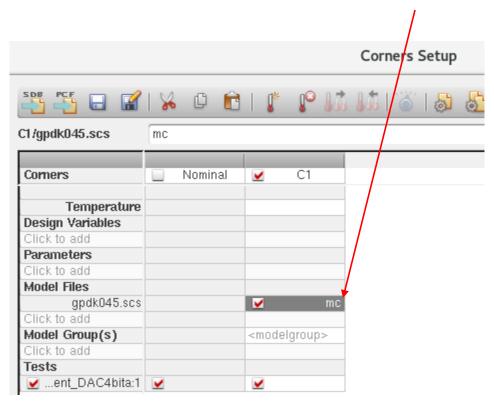De-select "Normal" and Select C1 and then choose "mc"




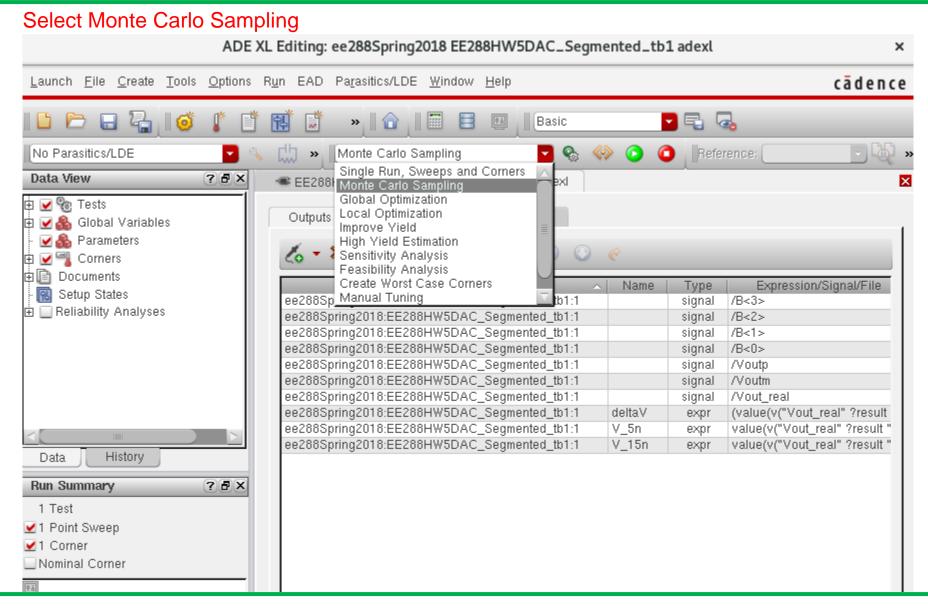

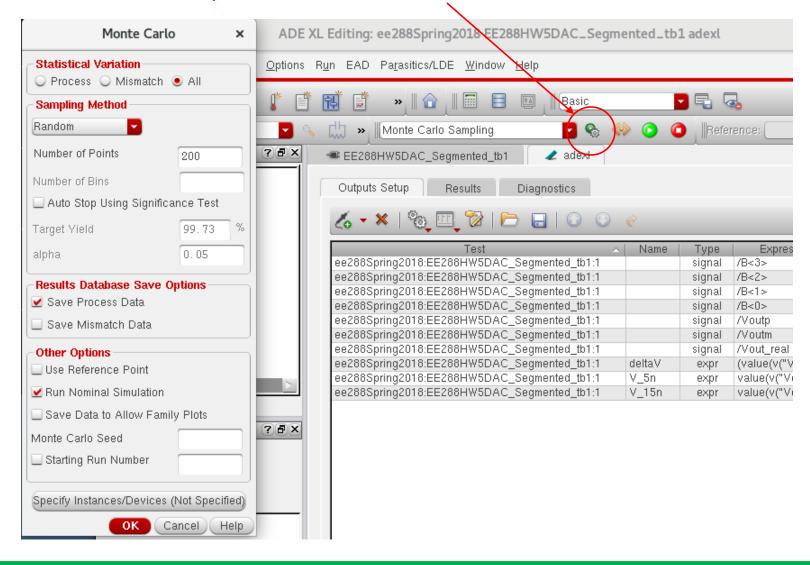Click the Monte Carlo setup icon and fill out the form




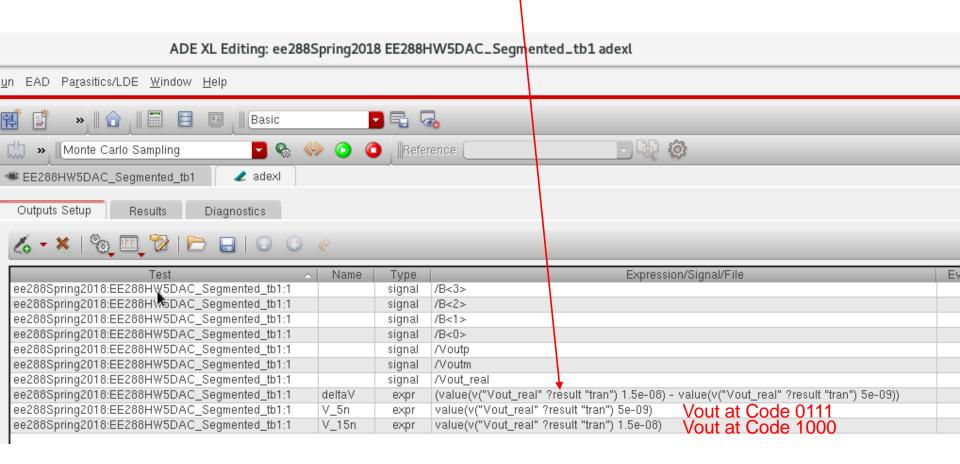Setup the result expression to calculate the DNL at major bit transition as shown below.



deltaV = DNL = Vout at Code 1000 - Vout at Code 1000

MC Simulation Result: Segmented DAC

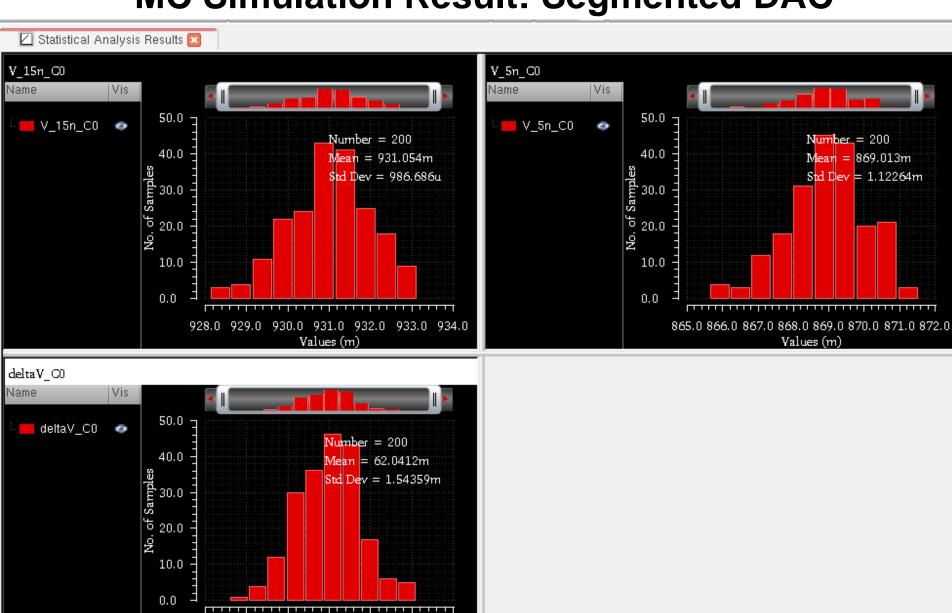

60.0

56.0

62.0

Values (m)

64.0

68.0

66.0

MC Simulation Result: Binary Weigted DAC



DAC Monte Carlo Simulation

Segmented vs Binary Weighted

