

EE288 – HW5 Report

4-bit DAC design

(using 45nm CMOS Technology)

Muhammad Aldacher
Student ID: 011510317


Overview

1. High-Swing Cascode Bias circuit
 - Circuit
 - Testbench
2. Current Mirror branches (1x, 2x, 4x, & 8x)
3. DAC circuits
 - Binary DAC
 - Segmented DAC
4. Monte Carlo Simulations
5. Transient Simulations
6. Results & Summary


(1)

High-Swing Cascode Bias Circuit

Circuit

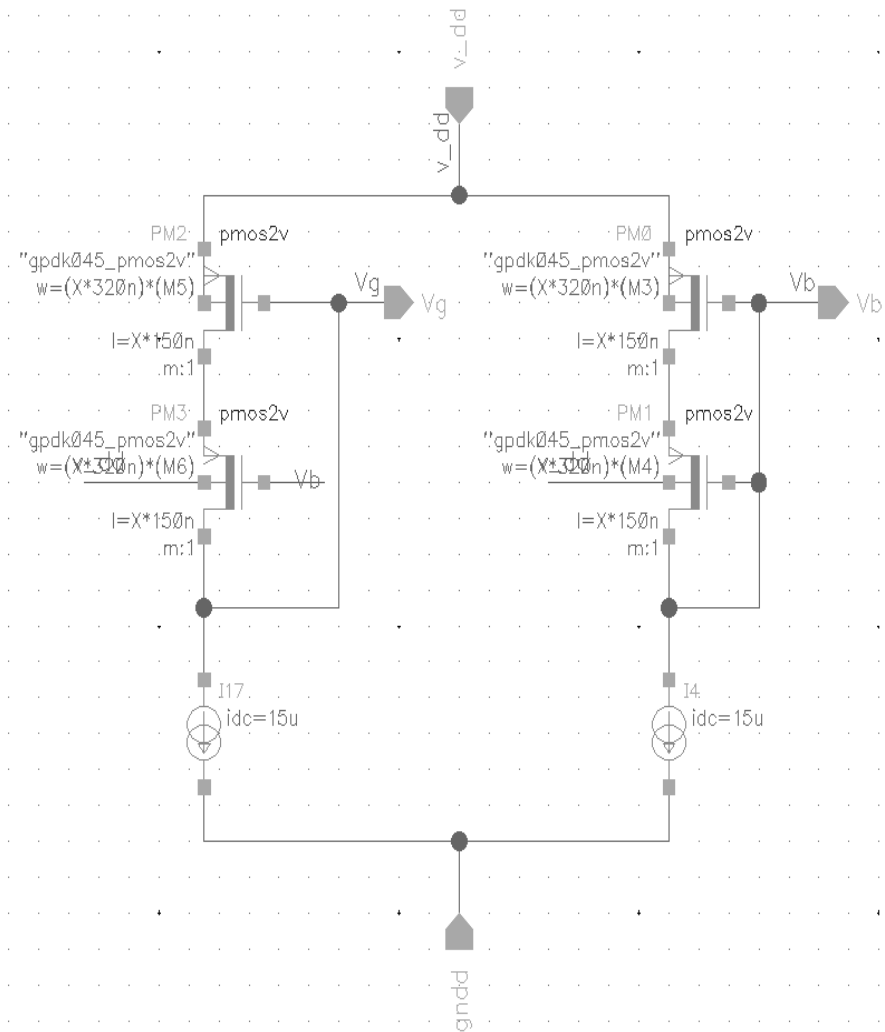

Testbench

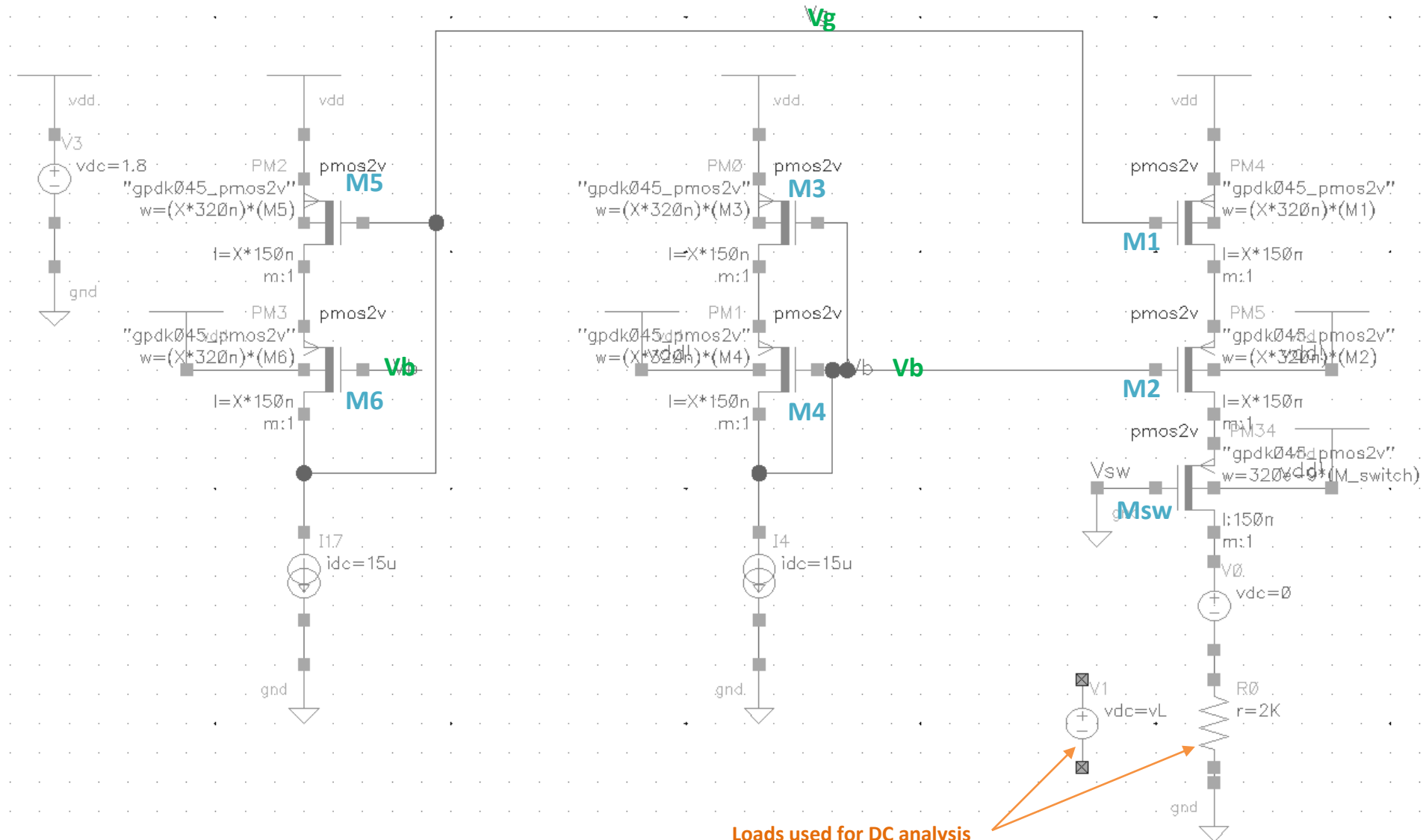

Testbench


- Sizing:

Device	Size (in terms of fingers, m)
M1	6
M2	5
M3	1
M4	5
M5	6
M6	5
Msw	4
Ideal Current Sources	15 μ A

- ➔ The aim is to have M1 & M2 in saturation with low V_{ds} . (V_{ds} of both transistors is monitored in the test)
- M2, M4, M6 are sized together to have equal current densities.
 - M3 is in triode. It's (W/L) is increased to decrease its V_{ds} , which will also be equal to V_{ds} of M5 & M1.
 - M5's (W/L) is increased to decrease V_g till M1 becomes in Saturation.
 - M1's (W/L) is then increased to provide a current of 15 μ A in the mirror branch.
 - M2 & Msw's sizes must ensure the passage of the 15 μ A in the mirror branch.
- In the testbench, besides using the 2K Ω load, a voltage source is used to make sure the mirror branch provides a 15 μ A at different output voltages (\sim 0.4v-1.4v).

Testbench


(for more than 1 mirror branch)

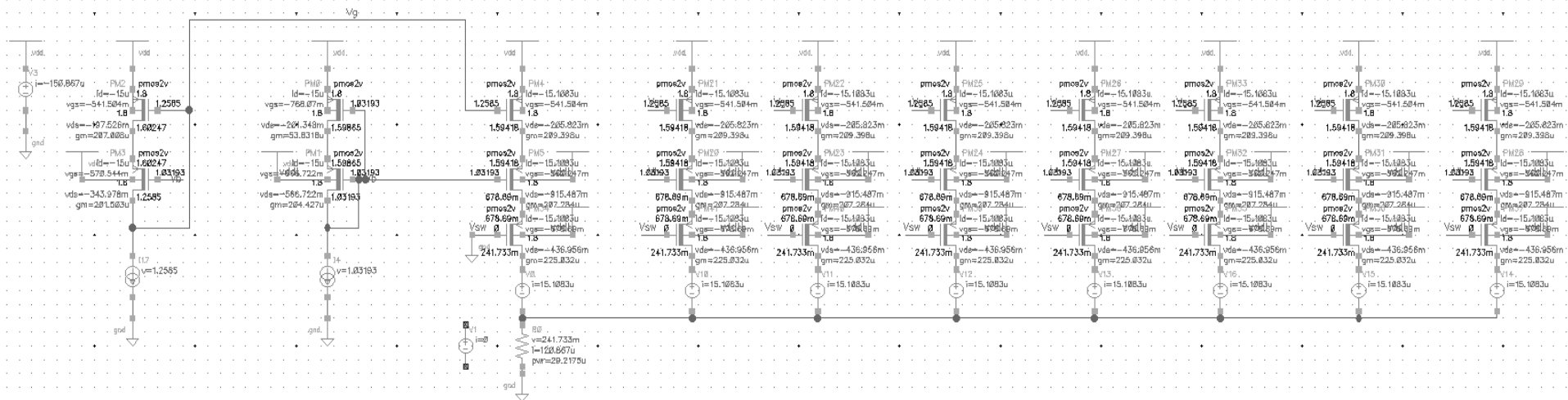


(2)

Current Mirror Branches


1x Current Mirror Branch

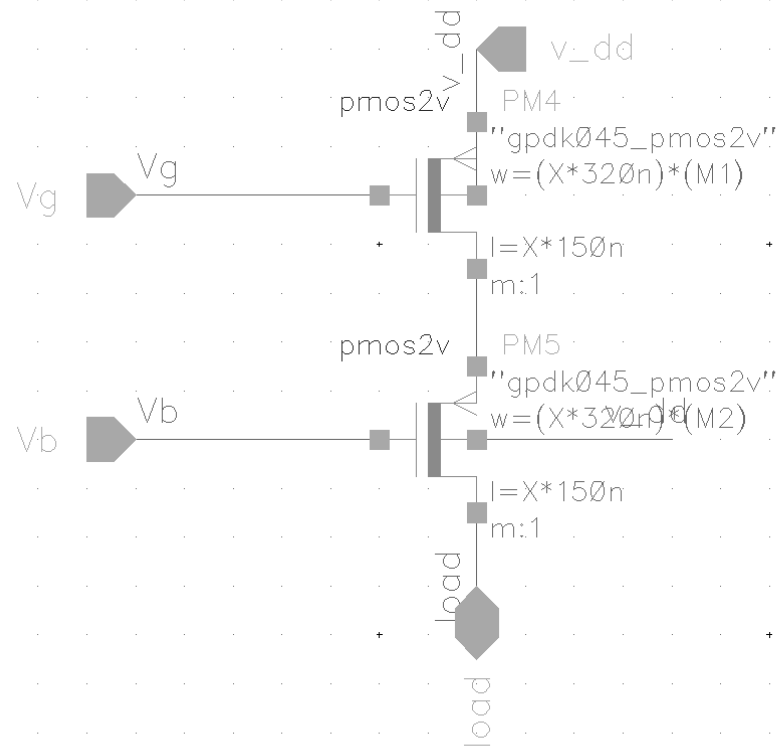


2x Current Mirror Branch

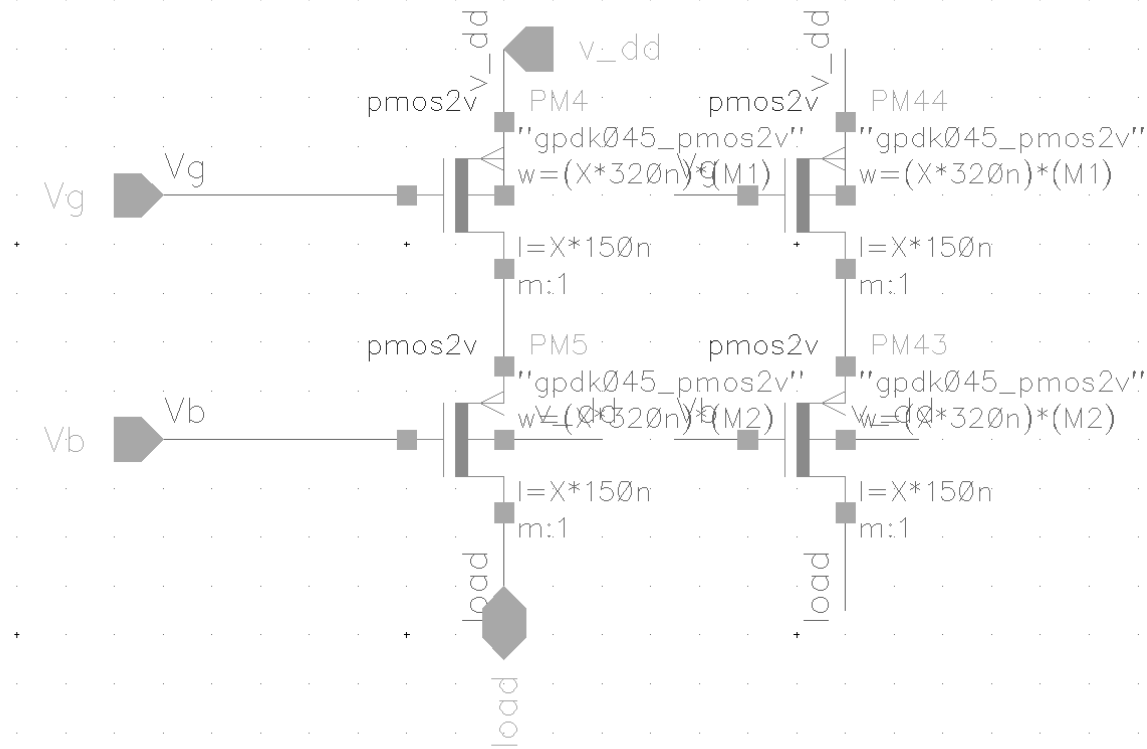

4x Current Mirror Branch

 


8x Current Mirror Branch

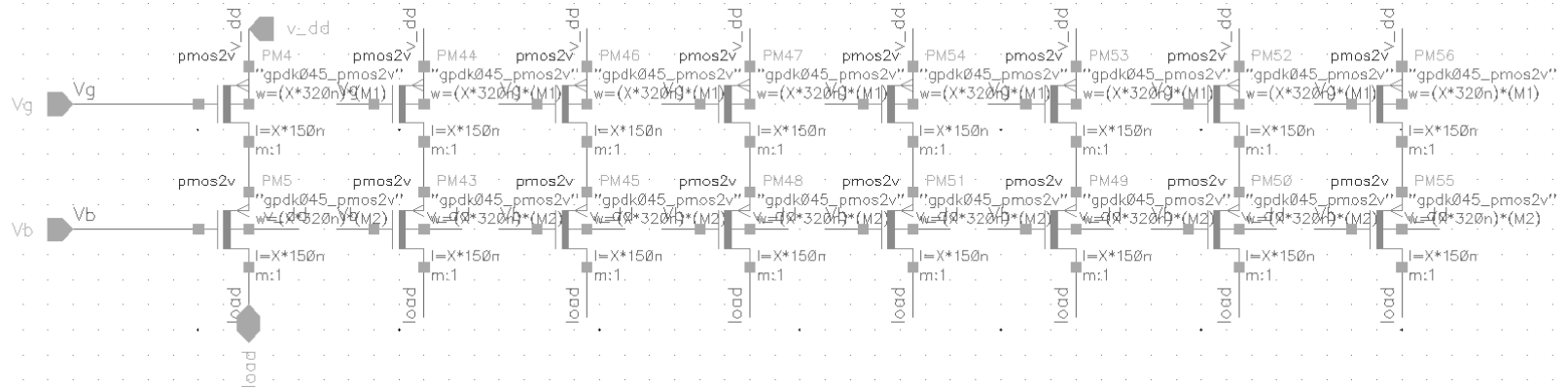


(3)

DAC Circuits

Binary DAC Circuit

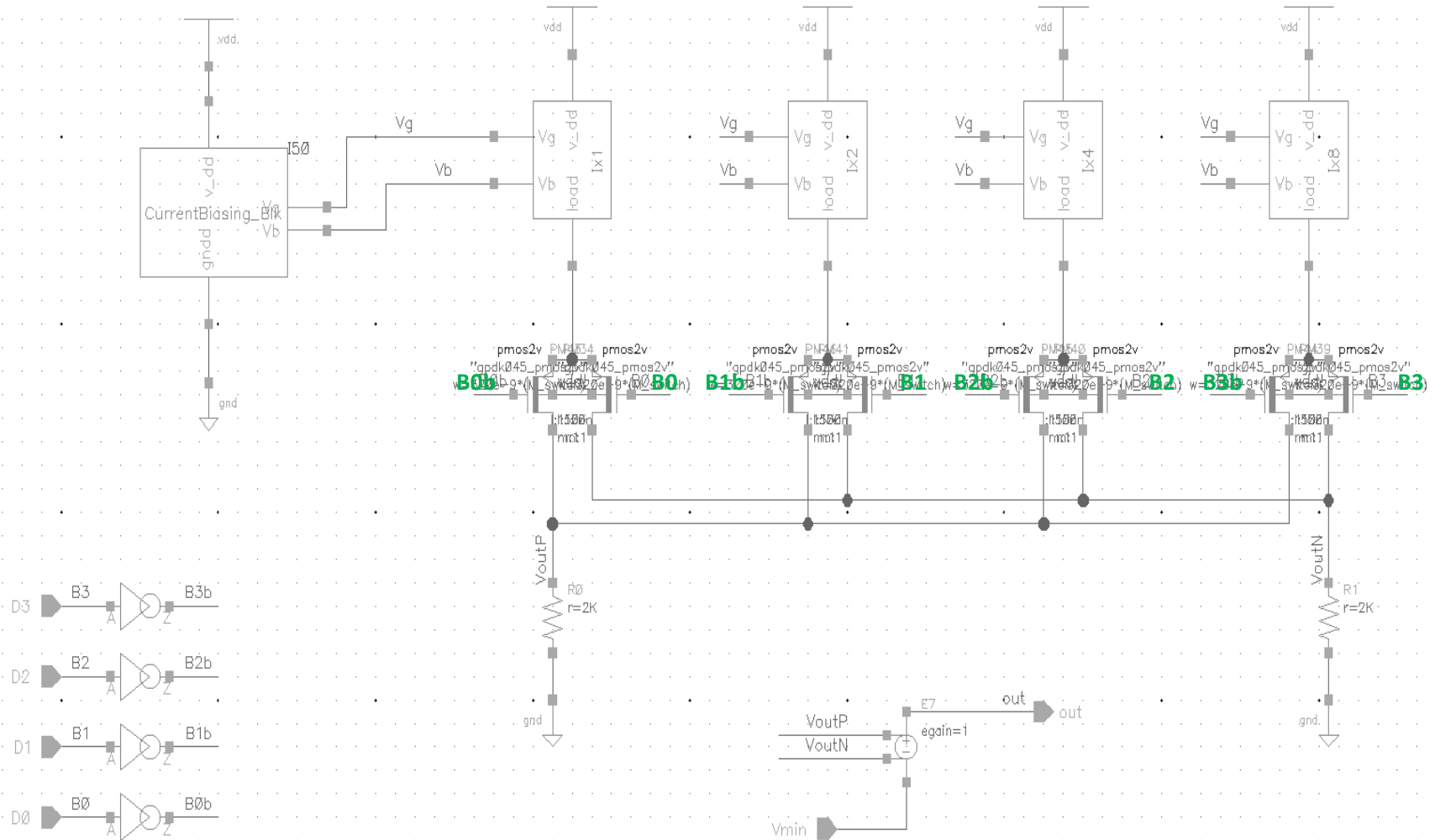

Segmented DAC Circuit

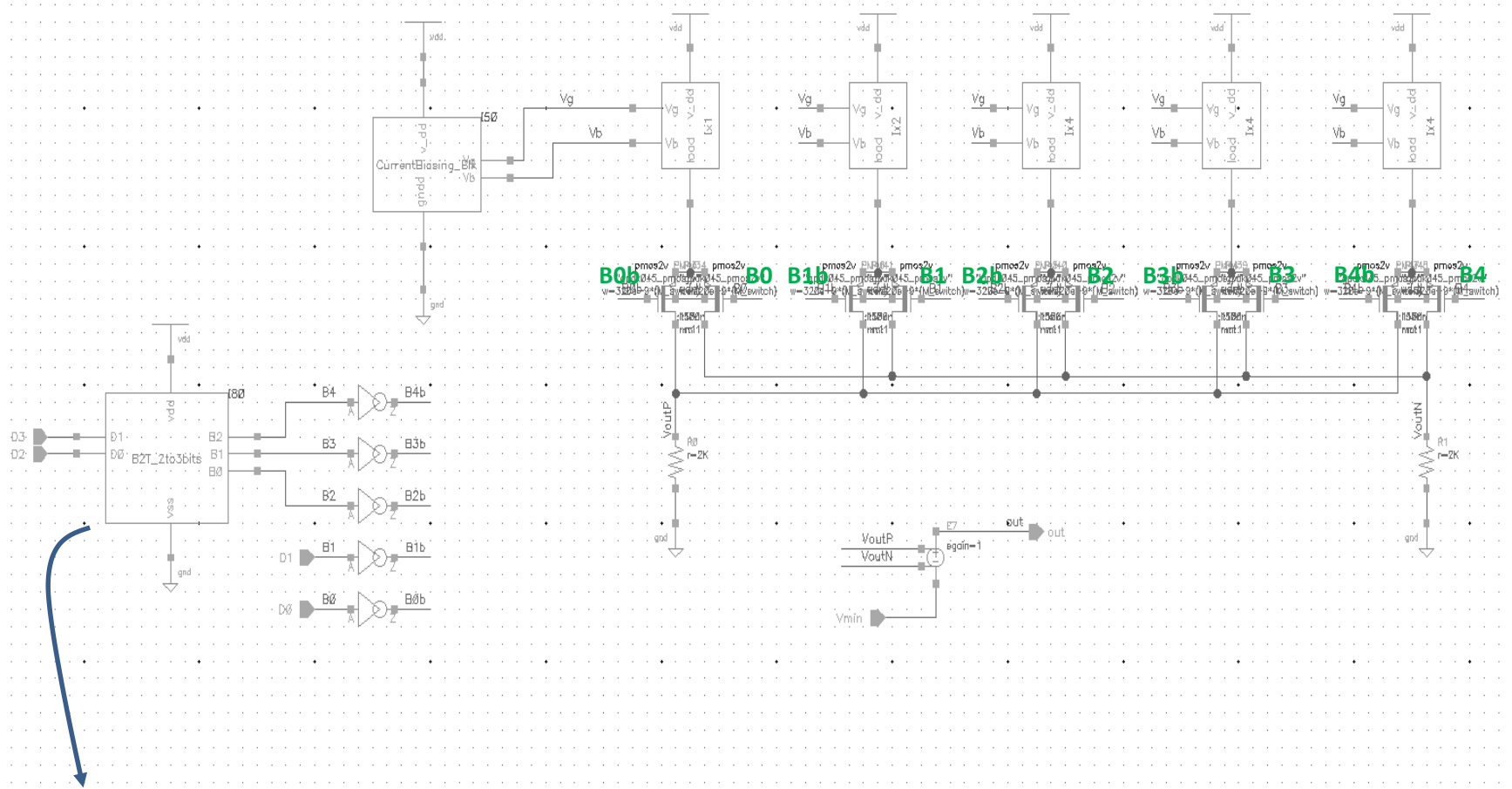

VerilogA:

BinaryToThermometer Block (2-to-3 bits)

```
// VerilogA for ADC_DACs, B2T_2to3bits, veriloga
```

```
`include "constants.vams"  
`include "disciplines.vams"
```

```
module B2T_2to3bits(D0,D1,B0,B1,B2,vdd,vss);
```

```
parameter real vtrans=0.5;  
parameter real delay = 0;  
parameter real ttime = 1p;
```

```
inout vdd,vss;  
input D0,D1;  
output B0,B1,B2;
```

```
electrical vdd,vss;  
electrical D0,D1;  
electrical B0,B1,B2;
```

```
real b_0,b_1,b_2;
```

```
analog begin
```

```
if ((V(D1)>0.9) && (V(D0)>0.9)) begin  
    b_2 = V(vdd);    b_1 = V(vdd);    b_0 = V(vdd);  
end
```

```
else if ((V(D1)>0.9) && (V(D0)<0.9)) begin  
    b_2 = V(vss);    b_1 = V(vdd);    b_0 = V(vdd);  
end
```

```
else if ((V(D1)<0.9) && (V(D0)>0.9)) begin  
    b_2 = V(vss);    b_1 = V(vss);    b_0 = V(vdd);  
end
```

```
else begin  
    b_2 = V(vss);    b_1 = V(vss);    b_0 = V(vss);  
end
```


```
V(B2) <+ transition(b_2,delay,ttime);  
V(B1) <+ transition(b_1,delay,ttime);  
V(B0) <+ transition(b_0,delay,ttime);
```

```
end  
endmodule
```


(4)

Monte Carlo Simulations


Testbench

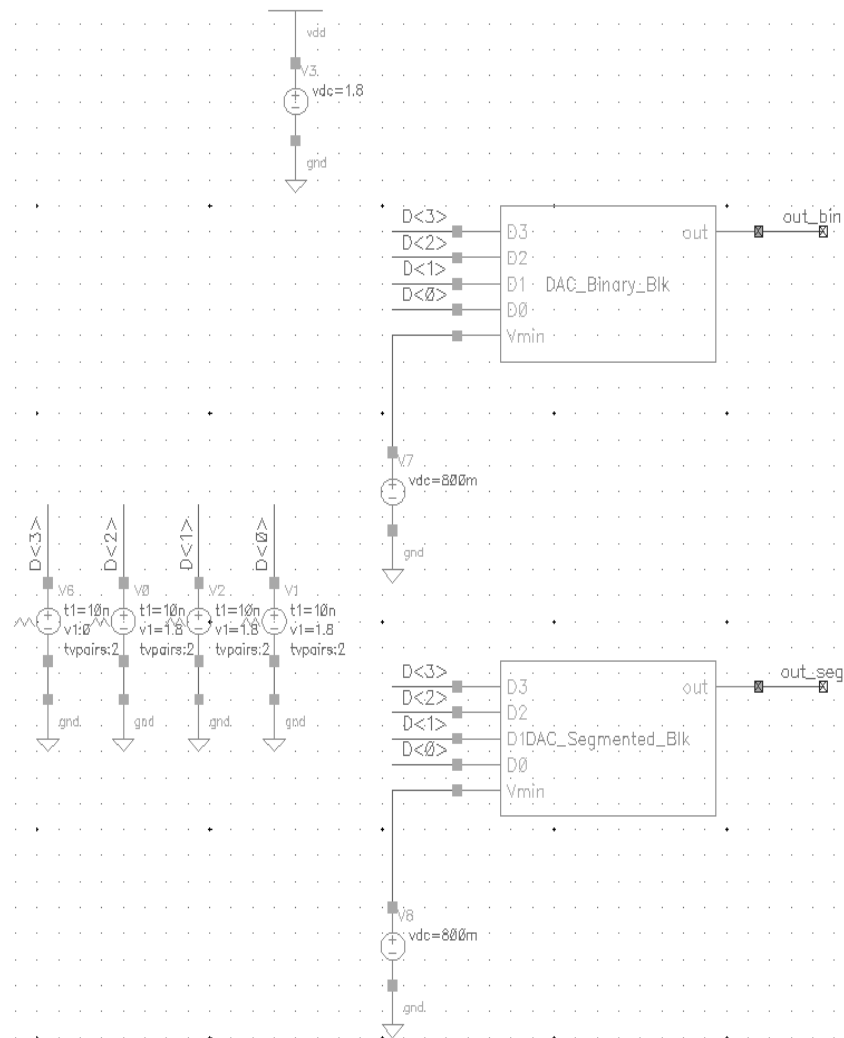



Transient Simulation

Transient Response


Mon Apr 16 23:30:30 2018

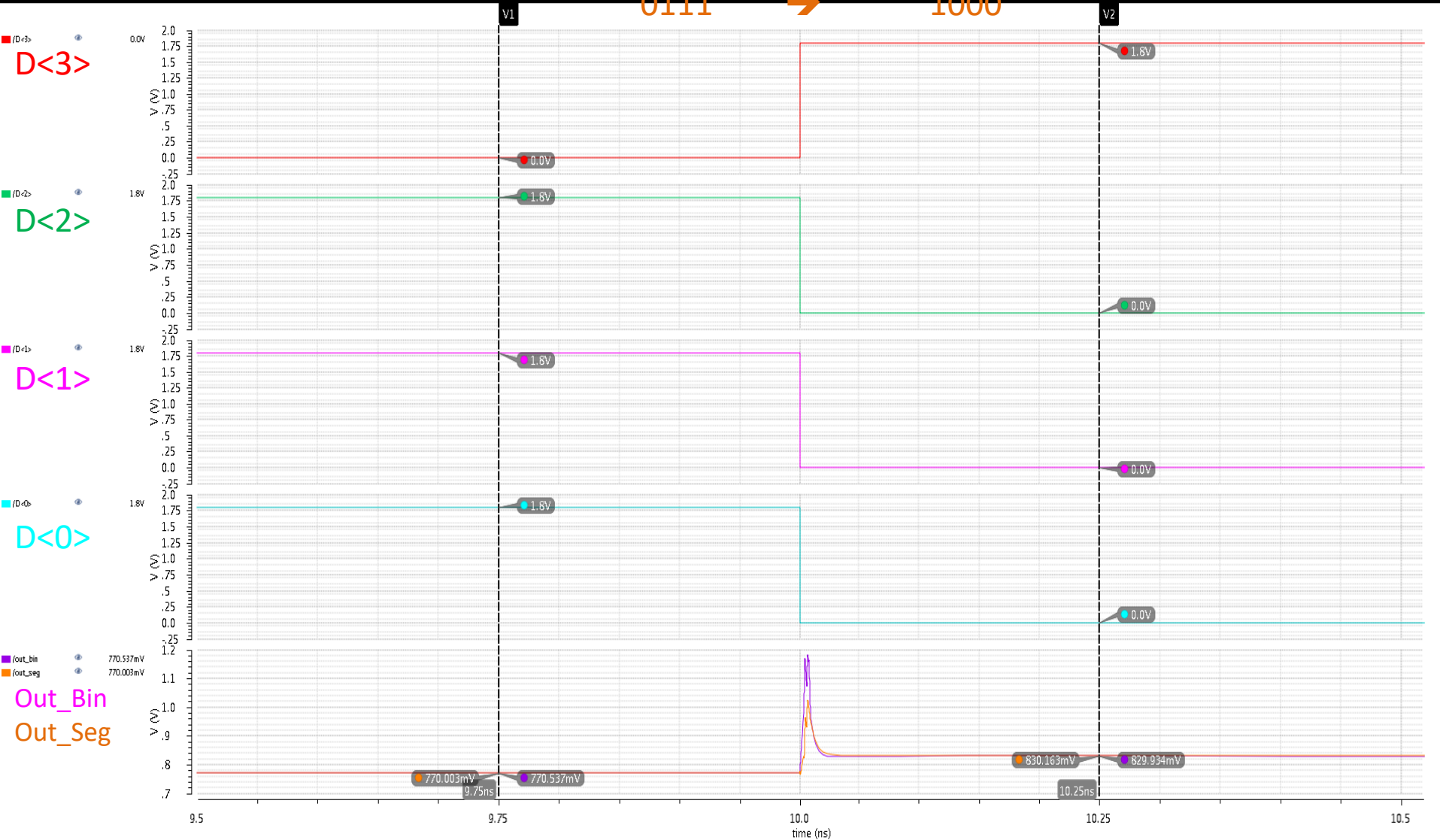



Monte Carlo Simulation (Binary DAC)

 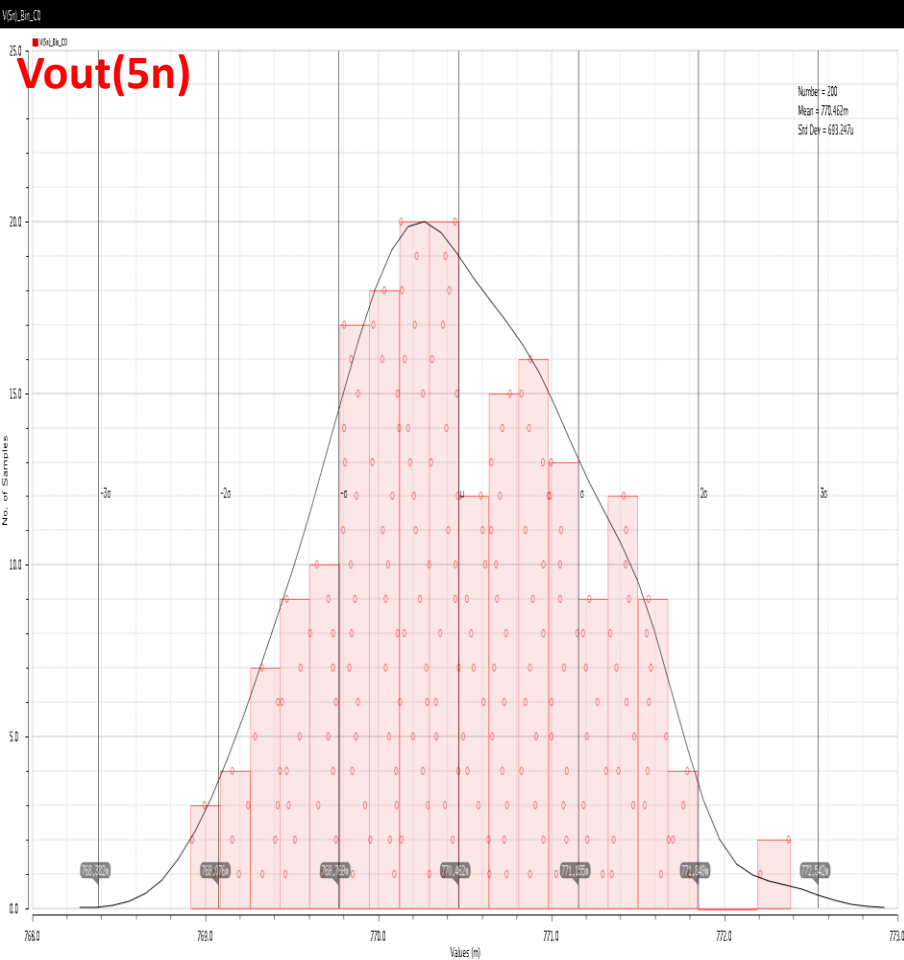


Monte Carlo Simulation (Binary DAC)

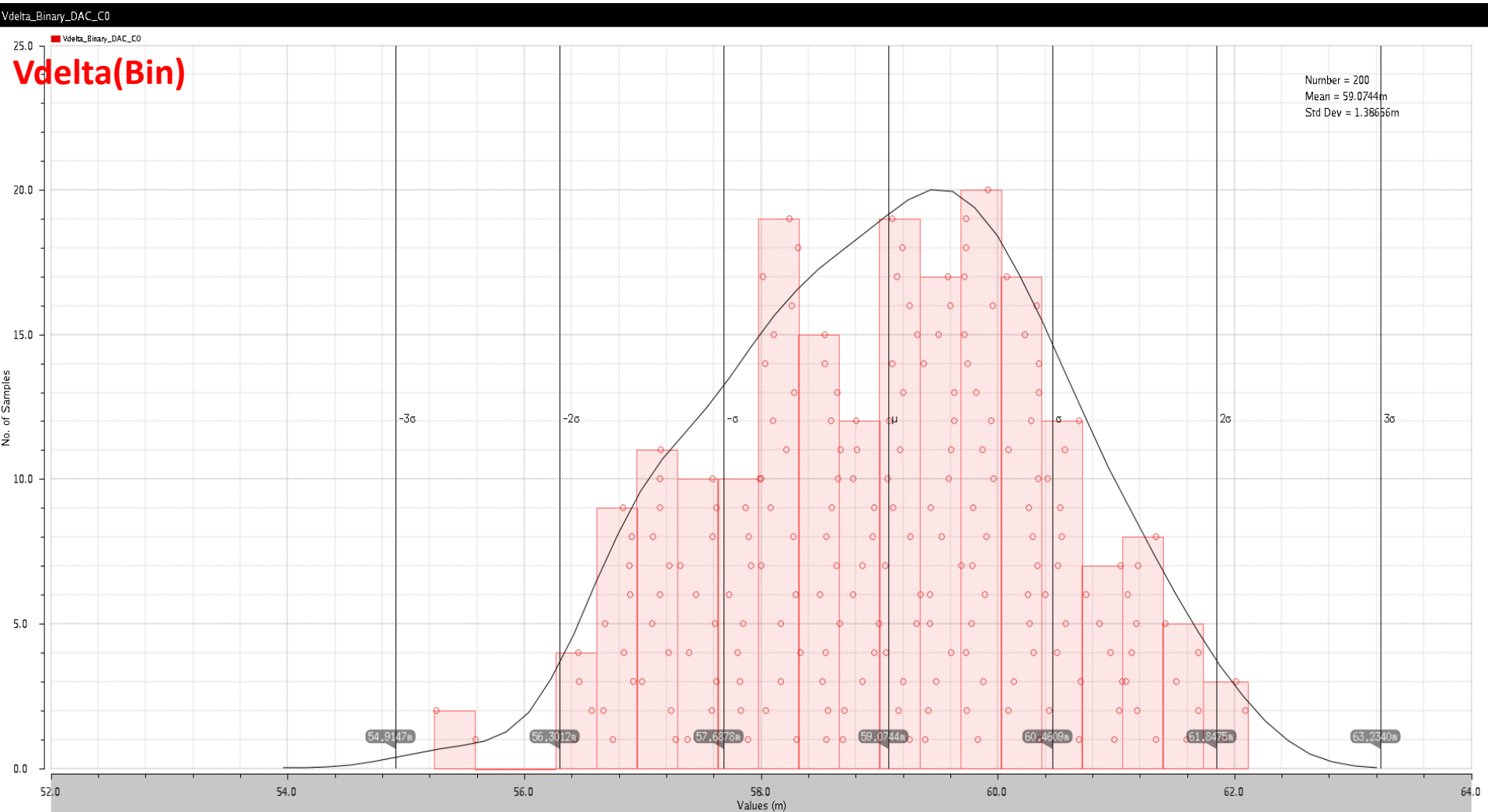



Monte Carlo Simulation (Segmented DAC)

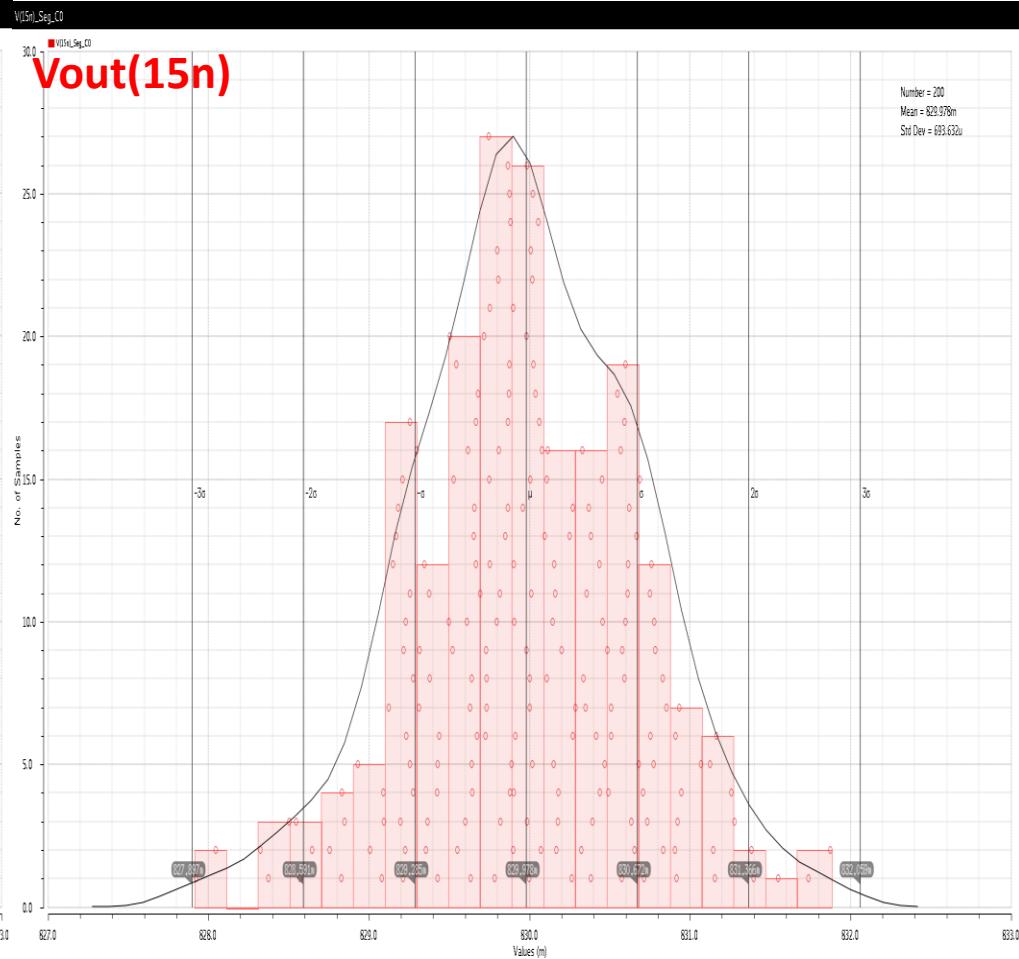 

Monte Carlo Simulation (Segmented DAC)

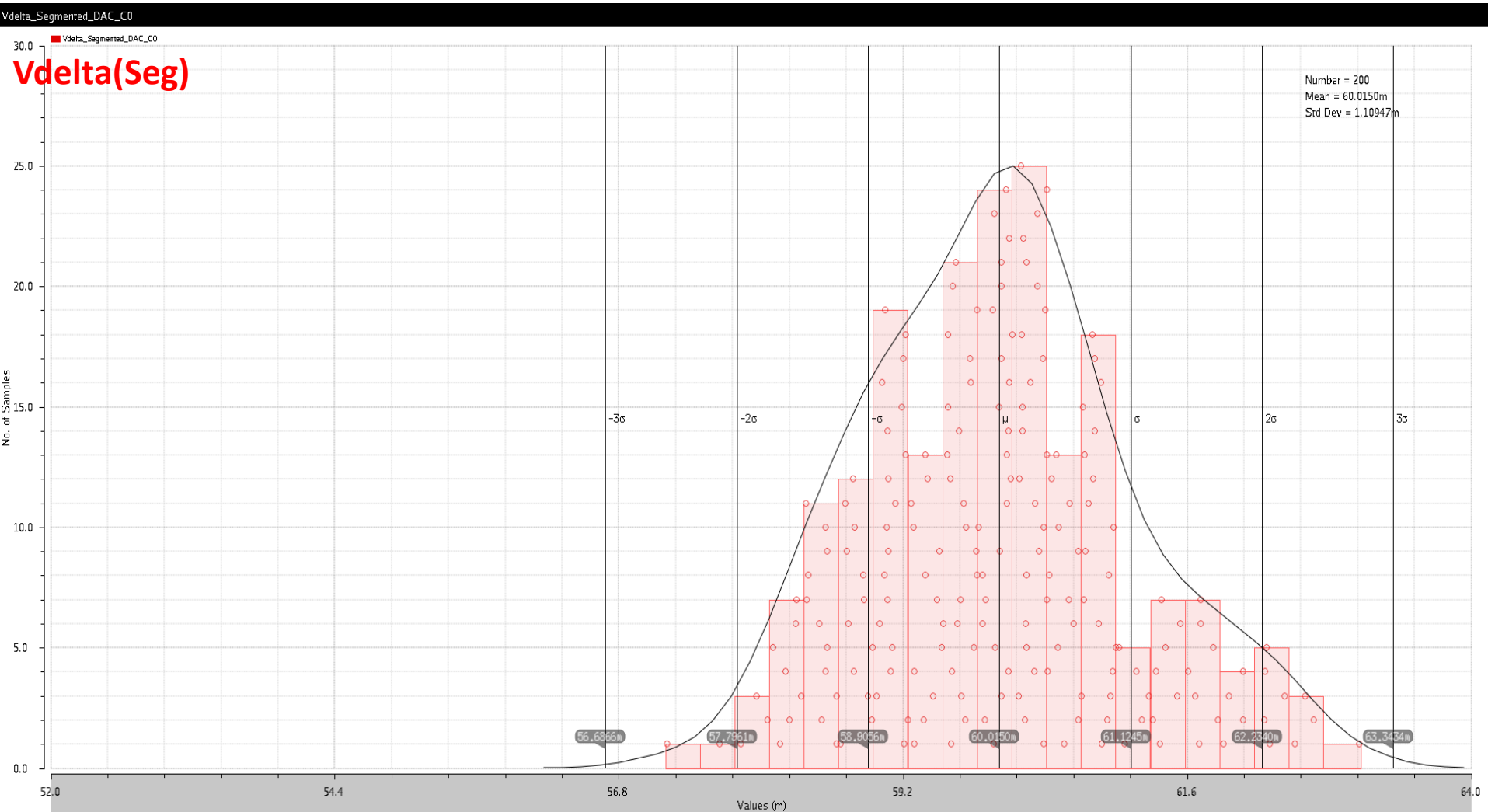

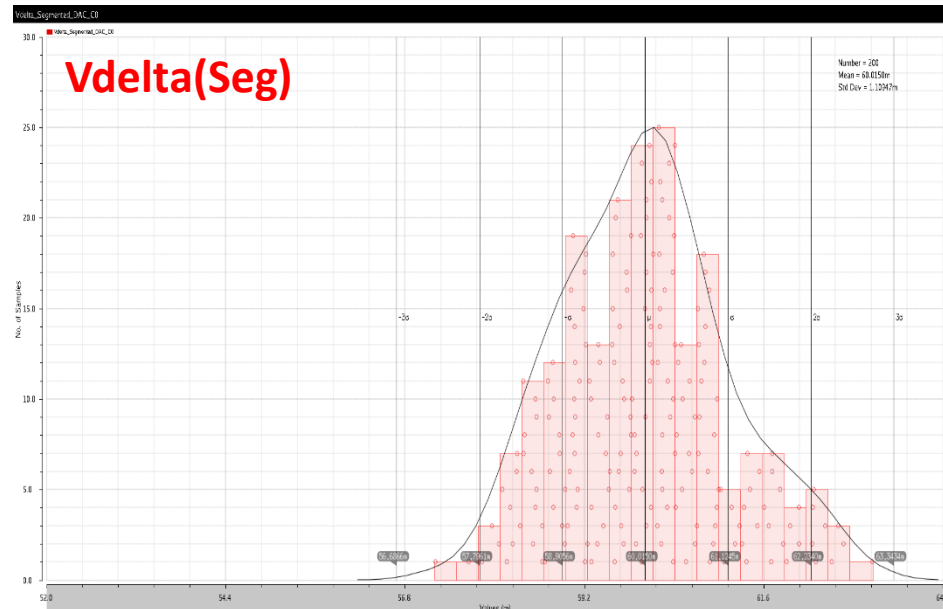 Monte Carlo Simulation (Binary DAC VS Segmented DAC)




Parameter	Binary DAC	Segmented DAC
Mean (μ)	59.074 mV	60.015 mV
Standard Deviation (σ)	1.3866 mV	1.1095 mV
5 σ	6.933 mV	5.548 mV
X	7	7

- Both $5 \cdot \sigma$ of the 2 DACs are less than 1/8 of 1 LSB ($\sim 7.8\text{mV}$) by choosing $X = 7$, which is the factor multiplied by all W s & L s of the Biasing & the Current Mirrors transistors.
- The standard deviation of the segmented DAC is smaller than that of the Binary DAC, giving better DNL performance.

(5)

Transient Simulations of
the Whole System


Whole System Testbench

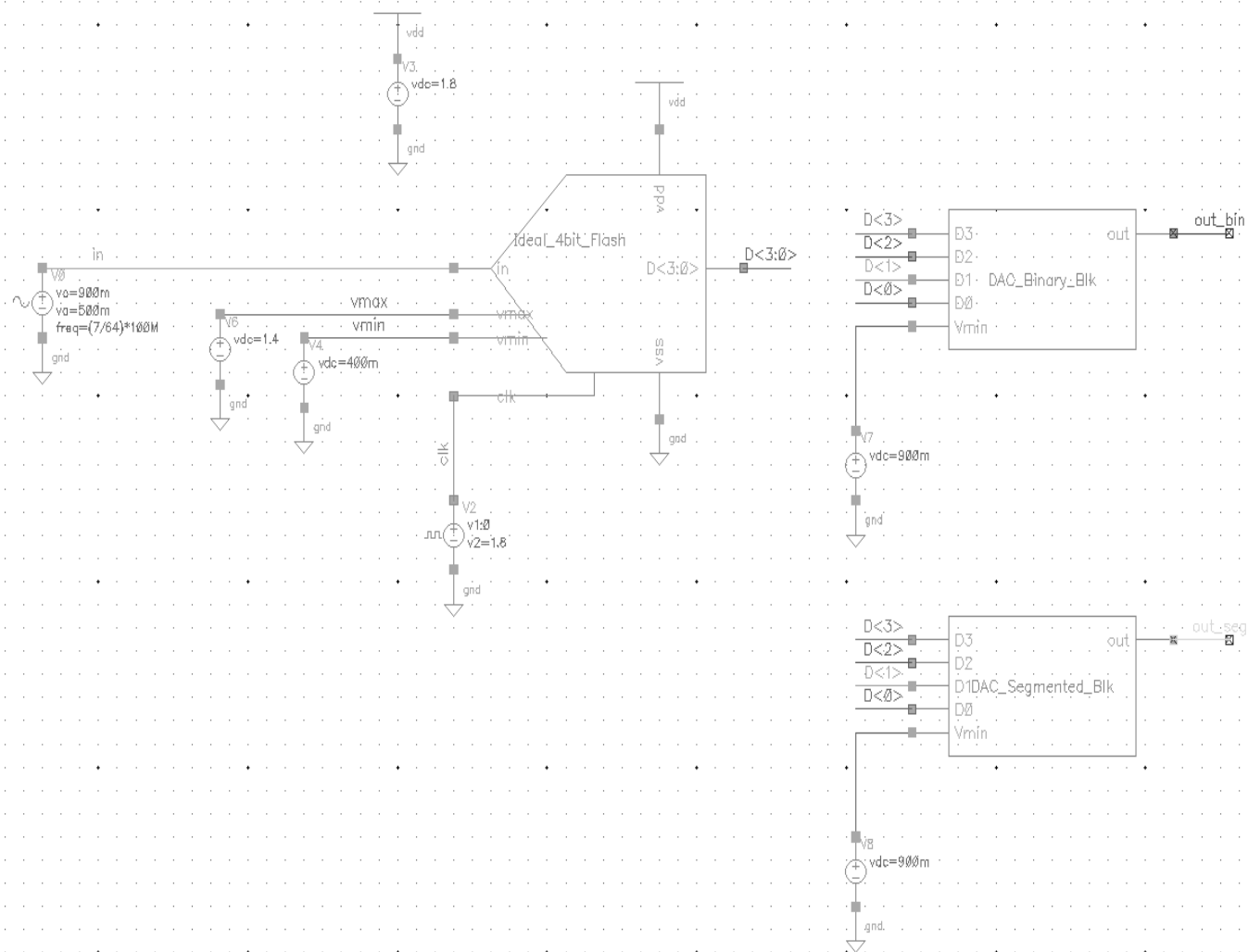

Waveforms

Transient Response

Sat Apr 21 00:58:53 2018

 

DFT of Binary DAC output


db20(dft(v("/out_bin" ?result "tran" 9n 649n 64 "Rectangular"))

Name

spectrum_out_bin

spectrum_out_bin

DFT of
Binary DAC
output

 

Measurement Value


out_bin	
ENOB	4.0234363 (bits)
SINAD	25.984086 (dB)
SNR	25.984086 (dB)
SFDR	31.545276 (dB)
THD	0 (%)
Signal ...	-6.5458679 (dB)
DC Po...	-1.9381933 (dB)
Noise F...	-47.581454 (dB)
Noise F...	-109.38177 (dB)

DFT of Segmented DAC output

db20(dft(v("/out_bin" ?result "tran") 9n 649n 64 "Rectangular"))

Name

 ■ spectrum_out_bin
■ spectrum_out_bin
**DFT of
Segmented
DAC output**



SUMMARY

Summary Notes:

- When designing the high-swing biasing circuit, it is important to size the transistors such that the current mirror transistors would have a small V_{ds} while also being in saturation, or else the variation seen in the Monte Carlo will be high.
- Increasing the W & L of the biasing & the current mirror circuits decreases the standard deviation observed in the Monte Carlo simulation, which means giving a better DNL performance.
- The Segmented DAC is shown to have smaller variation (standard deviation) than that in the Binary DAC.